

Power Supply Systems

Part II

Phase 8: Fuse and Protection

Aim: To learn fuse, HRC fuse, relay, circuit breaker, isolator and basic protection from absolute zero.

Style: Simple English, SN ma'am style, clean diagrams, no overlapping words, every diagram word explained.

Target: Definitions, diagrams, working, comparison tables, protection flow, time-current idea and semester-ready short notes.

Subject: Power Supply Systems

Section: Part II

Phase: 8 – Fuse and Protection

Level: Absolute zero to semester-question-ready

Contents


1 Phase 8 Roadmap	3
2 Need of Protection in Power System	3
3 Basic Protection Chain	4
4 Fuse	5
5 Simple Fuse Circuit Diagram	5
6 Working of Fuse	6
7 Important Fuse Terms	6
8 Fuse Operation Time Diagram	7
9 Desirable Properties of Fuse Element	7
10 Advantages and Disadvantages of Fuse	8
10.1 Advantages	8
10.2 Disadvantages	8
11 HRC Fuse	8
12 Construction of HRC Fuse	9
13 Clean Diagram of HRC Fuse	9
14 Working of HRC Fuse	9
15 HRC Fuse Working Flowchart	10
16 Advantages of HRC Fuse	10
16.1 Disadvantages of HRC Fuse	11
17 Time-Current Characteristic of Fuse	11
18 Protective Relay	12
19 Relay Protection Diagram	12
20 Essential Qualities of Protective Relay	13
21 Circuit Breaker	13
22 Circuit Breaker Working Sequence	14

23 Types of Circuit Breakers	14
24 Isolator	15
25 Circuit Breaker and Isolator Arrangement	15
26 Correct Operating Sequence	15
26.1 To Shut Down a Circuit	15
26.2 To Energise a Circuit	16
27 Comparison: Fuse and Circuit Breaker	16
28 Comparison: Relay and Circuit Breaker	16
29 Comparison: Circuit Breaker and Isolator	16
30 Important Small Numericals	17
30.1 Numerical 1: Fusing Factor	17
30.2 Numerical 2: Total Operating Time	17
30.3 Numerical 3: Prospective Current	17
31 Reverse Engineering of Semester Questions	18
32 Most Predictable Semester Questions from Phase 8	18
33 Exam Answer Templates	18
33.1 Template 1: Fuse Answer	19
33.2 Template 2: HRC Fuse Answer	19
33.3 Template 3: Relay and Circuit Breaker Answer	19
33.4 Template 4: Isolator Answer	20
34 Phase 8 Final Memory Sheet	20
35 Phase 8 Self-Test	20

1 Phase 8 Roadmap

Phase 8 Goal

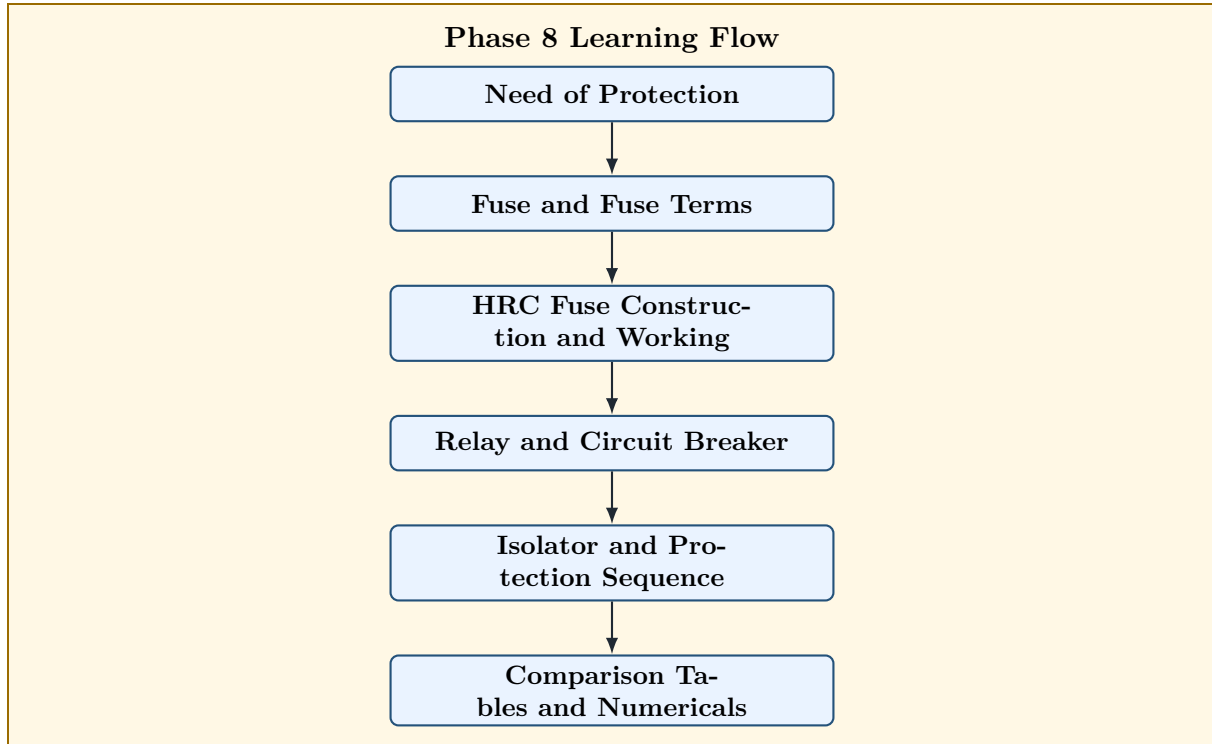After studying distributors, we must protect them. Phase 8 explains how faults are detected and removed using fuse, HRC fuse, relay, circuit breaker and isolator.



How to Read the Diagram

Word	Meaning
Need of Protection	Why electrical equipment must be protected from faults and overloads.
Fuse and Fuse Terms	Basic protective device and important terms like rated current, fusing current, prospective current and pre-arcing time.
HRC Fuse	High Rupturing Capacity fuse used for safely interrupting high fault currents.
Relay and Circuit Breaker	Relay detects abnormal condition; circuit breaker opens the faulty circuit.
Isolator	Mechanical switch used for isolation after the circuit is de-energised.
Comparison Tables and Numericals	Semester-ready differences and small calculations.

2 Need of Protection in Power System

Definition

Protection means the arrangement used to detect abnormal conditions and disconnect the faulty part from the healthy part of the power system.

Electrical faults may occur due to:

- short circuit,
- overload,
- insulation failure,
- earth fault,
- lightning,
- equipment failure,
- wrong operation.

Protection is needed to:

1. protect human life,
2. protect equipment from damage,
3. avoid fire,
4. reduce interruption time,
5. isolate only the faulty section,
6. maintain continuity of supply to healthy parts.


Memory Hook

Protection system does two jobs:

Detect fault

Disconnect faulty part

3 Basic Protection Chain

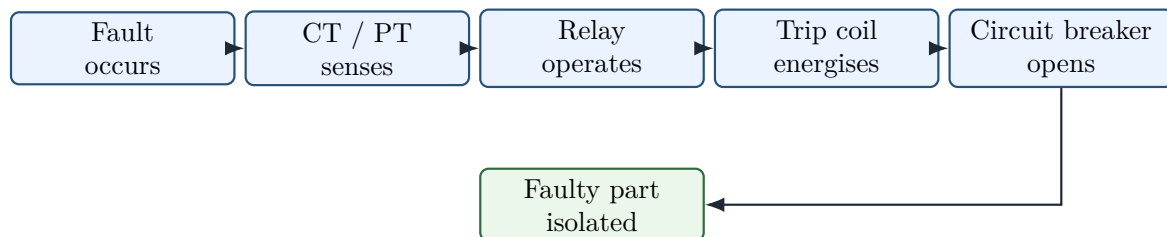

How to Read the Diagram

Word/Symbol	Meaning
Fault occurs	Abnormal condition like short circuit, earth fault or overload appears.
CT/PT senses	Current transformer or potential transformer gives safe signal to relay.
Relay operates	Relay detects abnormal current or voltage and closes its trip contact.
Trip coil energises	Trip coil of circuit breaker receives current and releases breaker mechanism.
Circuit breaker opens	The faulty circuit is disconnected automatically.
Faulty part isolated	Only the faulty section is separated from the healthy system.

4 Fuse


Definition

A **fuse** is a protective device having a short piece of metal which melts when excessive current flows through it and disconnects the circuit.

The metal piece inside the fuse is called the fuse element.

Fuse protects the circuit by melting under excessive current.

5 Simple Fuse Circuit Diagram

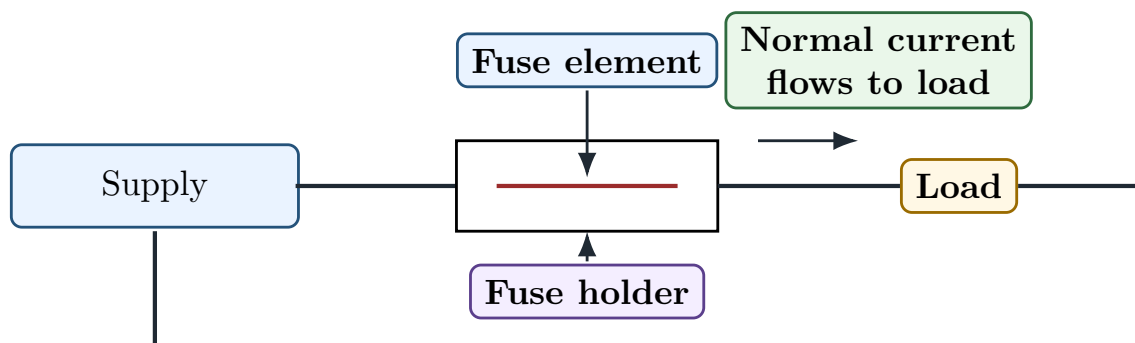

How to Read the Diagram

Word/Symbol	Meaning
Supply	Source of electrical energy.
Fuse holder	Insulating support which holds the fuse element.
Fuse element	Low melting point metal strip which melts during excessive current.
Load	Equipment connected to the supply.
Normal current	Current flowing safely during normal operation.
Return line	Path by which current returns to supply.

6 Working of Fuse

During normal condition:

$$I_{\text{load}} < I_{\text{fusing}}$$

The fuse element does not melt.

During overload or short circuit:

$$I_{\text{fault}} > I_{\text{fusing}}$$

Large heat is produced:

$$H \propto I^2 R t$$

The fuse element melts and opens the circuit.

Higher current $\Rightarrow$ more heat $\Rightarrow$ fuse melts faster

7 Important Fuse Terms


Term	Meaning
Fuse element	The metal part of fuse which melts during excessive current.
Current rating	Maximum current which the fuse can carry continuously without melting.
Fusing current	Minimum current at which the fuse element melts.
Fusing factor	Ratio of fusing current to current rating.
Cut-off current	Maximum instantaneous current reached before the fuse interrupts the circuit.
Prospective current	Fault current that would flow if the fuse were replaced by a solid conductor of negligible resistance.
Pre-arcing time	Time between start of fault and beginning of arc. It is the time taken by fuse element to melt.

Arcing time	Time from beginning of arc to complete arc extinction.
Total operating time	Sum of pre-arcing time and arcing time.
Breaking capacity	Maximum current that the fuse can safely interrupt at rated voltage.

$$\text{Fusing factor} = \frac{\text{Fusing current}}{\text{Current rating}}$$

$$\text{Total operating time} = \text{Pre-arcing time} + \text{Arcing time}$$

8 Fuse Operation Time Diagram

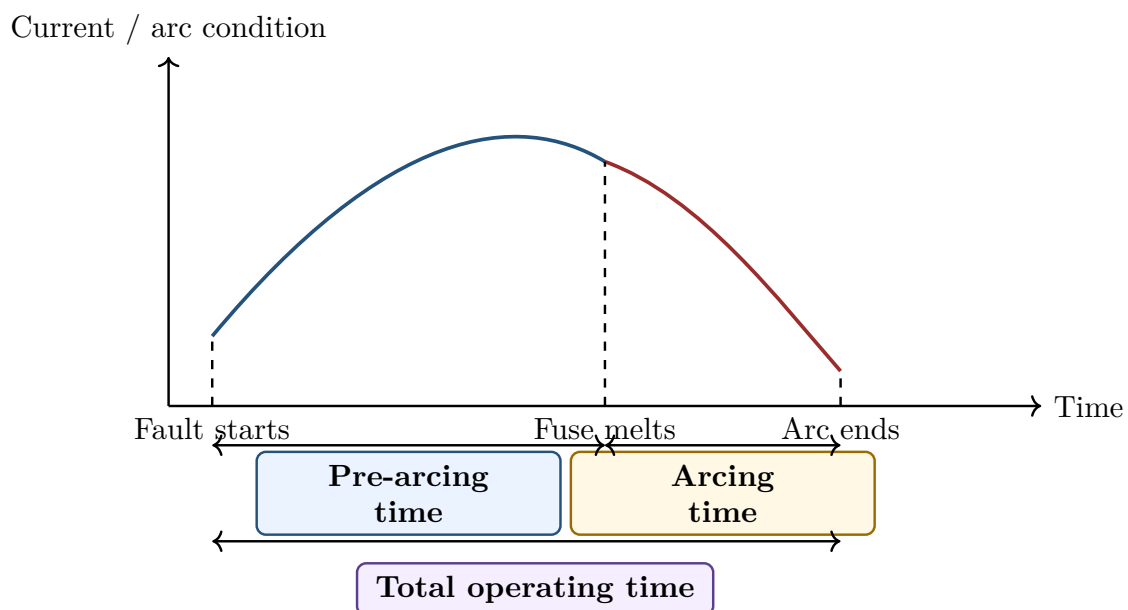

How to Read the Diagram

Word/Symbol	Meaning
Time	Horizontal axis showing time after fault starts.
Fault starts	Moment when abnormal current begins.
Fuse melts	Moment when fuse element becomes molten and arc begins.
Arc ends	Moment when arc is completely extinguished and circuit is interrupted.
Pre-arcing time	Time from fault start to melting of fuse element.
Arcing time	Time from fuse melting to final arc extinction.
Total operating time	Complete time taken by fuse to clear the fault.

9 Desirable Properties of Fuse Element

A good fuse element should have:

1. low melting point,
2. high conductivity,
3. low cost,
4. low deterioration due to oxidation,
5. stable characteristics,
6. suitable mechanical strength,
7. quick operation under fault.

Common fuse element materials are:

- tin,
- lead-tin alloy,
- silver,
- copper.

10 Advantages and Disadvantages of Fuse

10.1 Advantages

1. Simple and cheap.
2. Requires no maintenance.
3. Operates automatically.
4. Very fast under heavy fault.
5. Can interrupt large short-circuit current if properly rated.

10.2 Disadvantages

1. Fuse must be replaced after operation.
2. It cannot be used as a switch for repeated operation.
3. It has limited control flexibility.
4. Exact discrimination may be difficult.
5. It cannot be reset like a circuit breaker.

11 HRC Fuse

Definition

HRC fuse means **High Rupturing Capacity fuse**. It is a fuse designed to safely interrupt very high fault current without explosion or fire.

HRC fuse is used where high short-circuit current may occur.


HRC fuse = High Rupturing Capacity Fuse

12 Construction of HRC Fuse

An HRC fuse has:

1. ceramic body,
2. silver fuse element,
3. silica powder filling,
4. end caps,
5. terminal contacts,
6. striker pin in some types.

13 Clean Diagram of HRC Fuse

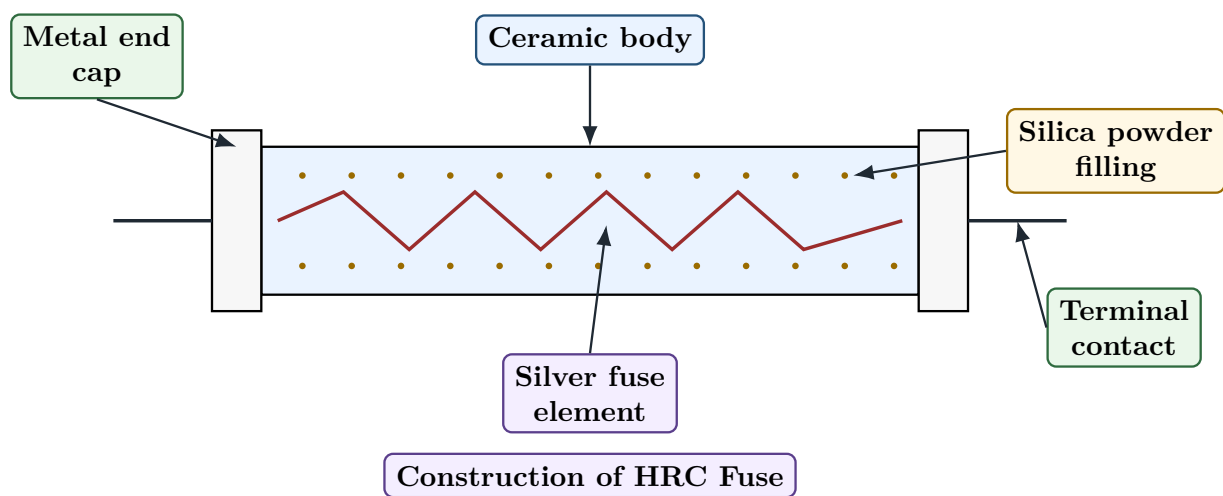

How to Read the Diagram

Word/Symbol	Meaning
Ceramic body	Strong insulating body which can withstand heat and pressure.
Silica powder filling	Filler material which absorbs heat and helps extinguish arc.
Silver fuse element	Conducting element which melts during fault current. Silver gives stable fuse characteristics.
Metal end cap	Conducting cap fitted at both ends of the fuse body.
Terminal contact	External connection point of the fuse.
Construction of HRC Fuse	Shows the internal parts of a cartridge type HRC fuse.

14 Working of HRC Fuse

During normal current, the silver element carries current safely.

During short circuit:

1. Very high current flows.


2. Fuse element melts at weak points.
3. Arc is produced.
4. Silica powder absorbs heat.
5. Silica changes into high-resistance glassy material.
6. Arc is extinguished quickly.
7. Faulty circuit is disconnected.

Memory Hook

In HRC fuse:

Fuse element melts → Arc forms → Silica absorbs heat → Arc extinguishes

15 HRC Fuse Working Flowchart

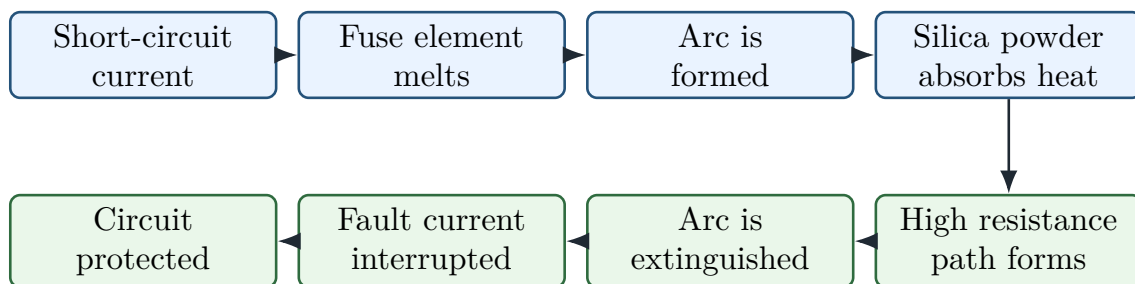

How to Read the Diagram

Step	Meaning
Short-circuit current	Very high current flows due to fault.
Fuse element melts	Silver fuse element melts due to I^2R heating.
Arc is formed	After melting, current continues for a short time through arc.
Silica powder absorbs heat	Silica absorbs arc heat and helps cooling.
High resistance path forms	Silica changes into glassy material and increases path resistance.
Arc is extinguished	The conducting arc is stopped.
Fault current interrupted	Fault current becomes zero.
Circuit protected	The faulty circuit is safely disconnected.

16 Advantages of HRC Fuse

1. High breaking capacity.
2. Fast operation during short circuit.
3. No smoke or flame.
4. Reliable and stable operation.

5. Requires less maintenance.
6. Good current-limiting property.
7. Compact size.

16.1 Disadvantages of HRC Fuse


1. It must be replaced after operation.
2. It cannot be used for frequent switching.
3. Characteristics cannot be adjusted like relay.
4. Initial cost is higher than simple rewirable fuse.

17 Time-Current Characteristic of Fuse

Definition

The **time-current characteristic** of a fuse shows the relation between current flowing through the fuse and the time taken by the fuse to operate.

Higher current causes faster operation.

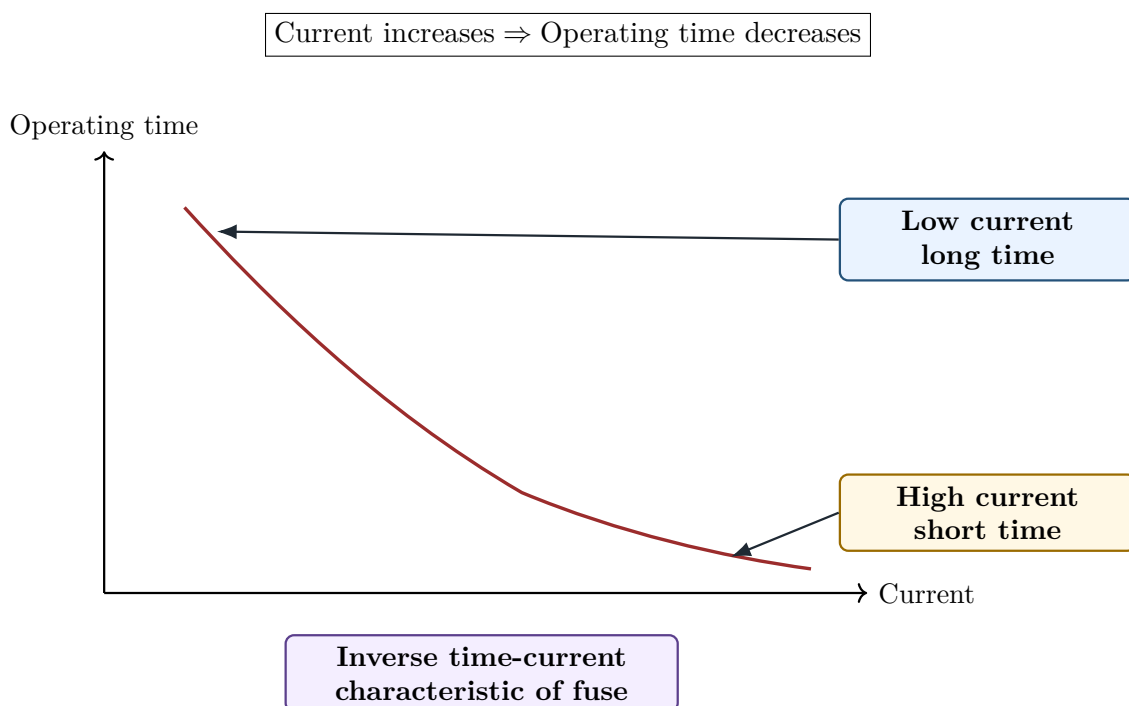

How to Read the Diagram

Word/Symbol	Meaning
Current	Horizontal axis. It shows current flowing through the fuse.
Operating time	Vertical axis. It shows time taken by fuse to clear the fault.
Low current long time	Slight overload may take longer time to melt the fuse.
High current short time	Heavy fault current melts the fuse very quickly.
Inverse characteristic	Operating time decreases as current increases.

18 Protective Relay


Definition

A **protective relay** is a device that detects abnormal conditions in an electrical circuit and causes the circuit breaker to trip.

Relay does not usually interrupt the main fault current directly. It senses fault and sends trip command to the circuit breaker.

Relay detects fault; circuit breaker clears fault.

19 Relay Protection Diagram

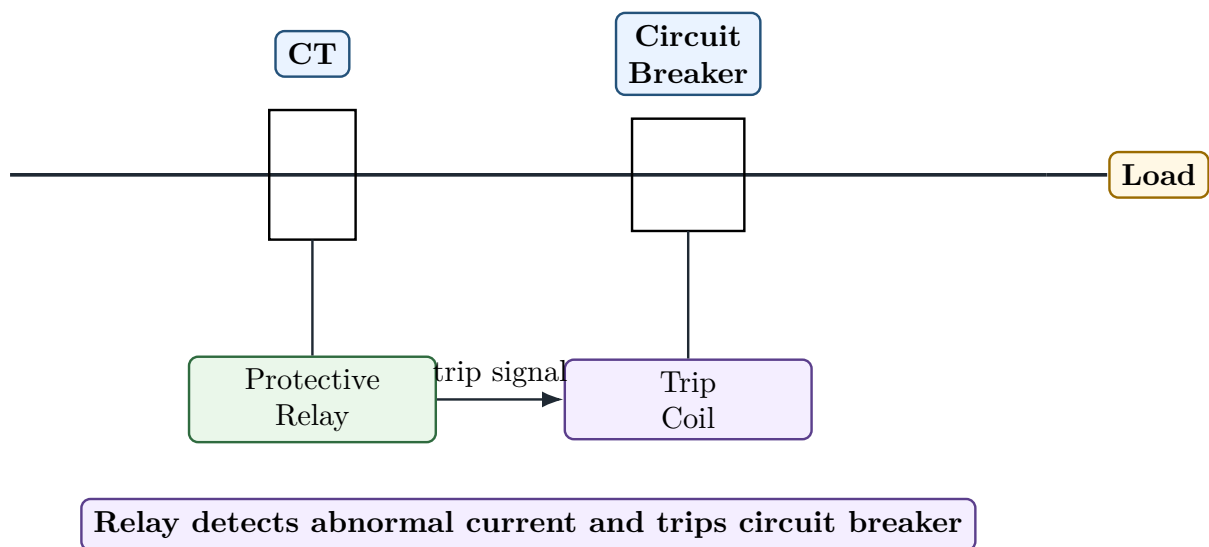

How to Read the Diagram

Word/Symbol	Meaning
Power line	Main circuit carrying load current.
CT	Current transformer. It gives reduced current signal to relay.
Protective Relay	Device which senses abnormal current and gives trip signal.
Trip signal	Electrical command sent from relay to trip coil.
Trip Coil	Coil which operates the circuit breaker tripping mechanism.
Circuit Breaker	Device which opens the main circuit and interrupts fault current.
Load	Consumer or equipment connected to the protected circuit.

20 Essential Qualities of Protective Relay

A good relay protection system should have:

1. Reliability,
2. Selectivity,
3. Sensitivity,
4. Speed,
5. Stability,
6. Simplicity,
7. Economy.

Quality	Meaning
Reliability	Relay must operate when it should and must not operate when it should not.
Selectivity	Only the faulty section should be disconnected.
Sensitivity	Relay should detect even small abnormal conditions.
Speed	Fault should be cleared quickly.
Stability	Relay should not operate for external faults or normal conditions.
Simplicity	Scheme should be easy to understand and maintain.
Economy	Protection cost should be reasonable.

21 Circuit Breaker

Definition

A **circuit breaker** is a switching device which can make, carry and break current under normal as well as abnormal fault conditions.


A circuit breaker can be opened:

- manually,

- automatically by relay operation.

Circuit breaker interrupts fault current.

22 Circuit Breaker Working Sequence

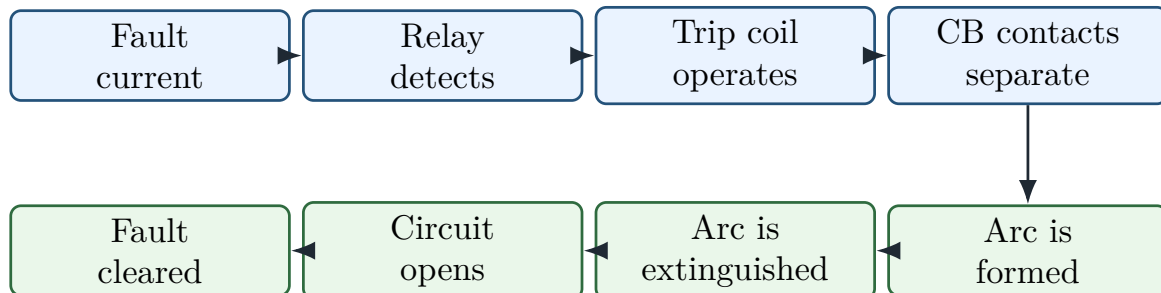

How to Read the Diagram

Step	Meaning
Fault current	Abnormally high current flows in the circuit.
Relay detects	Relay senses the abnormal condition through CT or PT.
Trip coil operates	Trip coil receives signal and releases breaker mechanism.
CB contacts separate	Main contacts of circuit breaker open.
Arc is formed	Current continues momentarily through arc between separating contacts.
Arc is extinguished	Breaker medium extinguishes the arc.
Circuit opens	Current path becomes open.
Fault cleared	Faulty part is disconnected from the system.

23 Types of Circuit Breakers

Common circuit breakers are:

1. Oil circuit breaker,
2. Air blast circuit breaker,
3. SF₆ circuit breaker,
4. Vacuum circuit breaker,
5. Miniature circuit breaker,
6. Moulded case circuit breaker.

Type	Main Idea
Oil circuit breaker	Oil is used for insulation and arc extinction.
Air blast circuit breaker	High-pressure air blast extinguishes arc.
SF ₆ circuit breaker	Sulphur hexafluoride gas is used for arc extinction.

Vacuum circuit breaker	Contacts open in vacuum; arc is quickly extinguished.
MCB	Low-voltage automatic protective switch for small circuits.
MCCB	Low-voltage breaker for higher current circuits than MCB.

24 Isolator

Definition


An **isolator** is a mechanical switch used to isolate a part of the circuit after the circuit has been made dead.

Important point:

Isolator should not be opened on load.

It is used only after circuit breaker has opened the circuit.

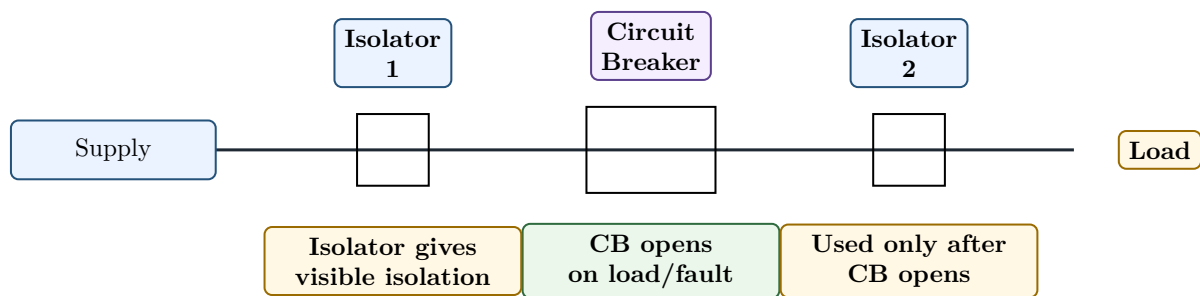25 Circuit Breaker and Isolator Arrangement



How to Read the Diagram

Word/Symbol	Meaning
Supply	Source side of the circuit.
Load	Equipment receiving power.
Isolator 1 and Isolator 2	Mechanical switches used for visible isolation during maintenance.
Circuit Breaker	Device capable of interrupting load current and fault current.
CB opens on load/fault	Circuit breaker can safely open current-carrying circuit.
Visible isolation	Isolator gives clear physical separation after circuit is dead.
Used only after CB opens	Isolator must not be opened while current is flowing.

26 Correct Operating Sequence

26.1 To Shut Down a Circuit

Open circuit breaker first

Then open isolators

26.2 To Energise a Circuit

Close isolators first

Then close circuit breaker

Memory Hook

Remember:

CB handles current. Isolator handles isolation.

27 Comparison: Fuse and Circuit Breaker

Point	Fuse	Circuit Breaker
Function	Protects by melting	Protects by opening contacts
Operation	Automatic only	Manual and automatic
Replacement	Must be replaced after operation	Can be reset after operation
Cost	Cheaper	Costlier
Maintenance	Very low	Requires maintenance
Control	No remote control generally	Remote and automatic control possible
Use	Low and medium protection applications	Repeated switching and fault clearing

28 Comparison: Relay and Circuit Breaker

Point	Relay	Circuit Breaker
Main job	Detects fault	Interrupts fault current
Current handling	Handles small signal current	Handles main circuit current
Connection	Connected through CT/PT	Connected in main power circuit
Output	Sends trip command	Opens circuit contacts
Can clear fault alone?	No	Yes, after trip command

29 Comparison: Circuit Breaker and Isolator

Point	Circuit Breaker	Isolator
Purpose	Interrupts current	Provides isolation
Operation on load	Can operate on load	Should not operate on load

Arc extinction	Has arc extinction system	No arc extinction system
Automatic operation	Possible through relay	Generally manual
Use	Protection and switching	Maintenance isolation
Operating sequence	Open first during shutdown	Open after circuit breaker

30 Important Small Numericals

30.1 Numerical 1: Fusing Factor

Problem: A fuse has current rating of 20 A and fusing current of 30 A. Find fusing factor.

Solution:

$$\begin{aligned}\text{Fusing factor} &= \frac{\text{Fusing current}}{\text{Current rating}} \\ &= \frac{30}{20}\end{aligned}$$

$$\boxed{\text{Fusing factor} = 1.5}$$

30.2 Numerical 2: Total Operating Time

Problem: A fuse has pre-arcing time 0.02 s and arcing time 0.01 s. Find total operating time.

Solution:

$$\begin{aligned}\text{Total operating time} &= \text{Pre-arcing time} + \text{Arcing time} \\ &= 0.02 + 0.01\end{aligned}$$

$$\boxed{\text{Total operating time} = 0.03 \text{ s}}$$

30.3 Numerical 3: Prospective Current

Problem: A supply voltage is 250 V and total fault path impedance is 0.05Ω. Find prospective current.

Solution:

$$\begin{aligned}I_{\text{prospective}} &= \frac{V}{Z} \\ I_{\text{prospective}} &= \frac{250}{0.05}\end{aligned}$$

$$\boxed{I_{\text{prospective}} = 5000 \text{ A}}$$

Semester Answer Style

Prospective current means the fault current that would flow if the protective device did not interrupt the circuit.

31 Reverse Engineering of Semester Questions

Syllabus Word	Concept	Semester Question Form
Fuse	Melting protective device	Define fuse and explain working with diagram.
Fuse terms	Rated current, fusing current, fusing factor	Define prospective current, pre-arcing time, arcing time.
HRC fuse	High rupturing capacity fuse	Draw and explain construction and working of HRC fuse.
Protection	Detect and isolate fault	Draw protection flow using relay and circuit breaker.
Protective relay	Fault detecting device	Define relay and list qualities of protective relay.
Circuit breaker	Fault current interrupting device	Explain working sequence of circuit breaker.
Isolator	Off-load mechanical isolation switch	Difference between circuit breaker and isolator.
Comparison	Fuse vs CB, relay vs CB	Write comparison tables.

32 Most Predictable Semester Questions from Phase 8

No.	Question	Marks
1	Define fuse. Explain its working with a neat diagram.	4–5
2	Define current rating, fusing current and fusing factor.	3–4
3	Define prospective current, pre-arcing time, arcing time and breaking capacity.	4–6
4	Draw and explain construction of HRC fuse.	5–6
5	Explain working of HRC fuse.	5
6	Draw time-current characteristic of fuse and explain.	4
7	What is protective relay? Mention essential qualities of protective relay.	5
8	Draw basic relay-circuit breaker protection scheme and explain.	5–6
9	Define circuit breaker. Explain its working sequence.	4–5
10	Differentiate between fuse and circuit breaker.	4–6
11	Differentiate between circuit breaker and isolator.	4–6
12	Explain correct operating sequence of circuit breaker and isolator.	3–4

33 Exam Answer Templates

33.1 Template 1: Fuse Answer

Semester Answer Style

Answer sequence:

1. Define fuse.
2. Draw simple fuse circuit diagram.
3. Label fuse element, fuse holder, supply and load.
4. Explain normal operation.
5. Explain fault operation using I^2R heating.
6. Write advantages and disadvantages.

33.2 Template 2: HRC Fuse Answer

Semester Answer Style

Answer sequence:

1. Write full form: High Rupturing Capacity.
2. Draw construction diagram.
3. Label ceramic body, silver element, silica powder, end caps and terminals.
4. Explain working during fault.
5. Write advantages.

33.3 Template 3: Relay and Circuit Breaker Answer

Semester Answer Style

Answer sequence:

1. Define protective relay.
2. Define circuit breaker.
3. Draw CT–Relay–Trip Coil–CB diagram.
4. Explain that relay detects fault.
5. Explain that circuit breaker interrupts fault current.
6. Write qualities of relay or comparison if asked.

33.4 Template 4: Isolator Answer

Semester Answer Style

Answer sequence:

1. Define isolator.
2. State that isolator should not be opened on load.
3. Draw CB and isolator arrangement.
4. Write shutdown sequence:
Open CB first, then open isolator.
5. Write energising sequence:
Close isolator first, then close CB.

34 Phase 8 Final Memory Sheet

One-Page Memory Sheet

1. Protection detects faults and disconnects faulty parts.
2. Fuse protects by melting during excessive current.
3. Heating in fuse:
$$H \propto I^2 R t$$
4. Fusing factor:
$$\text{Fusing factor} = \frac{\text{Fusing current}}{\text{Current rating}}$$
5. Total operating time:
$$t_{\text{total}} = t_{\text{pre-arcing}} + t_{\text{arcing}}$$
6. Prospective current is the fault current that would flow if fuse did not interrupt.
7. HRC fuse means High Rupturing Capacity fuse.
8. In HRC fuse, silica powder helps arc extinction.
9. Relay detects fault and gives trip command.
10. Circuit breaker interrupts fault current.
11. Isolator gives visible isolation and should not be opened on load.
12. Shutdown sequence:

Open CB first, then open isolator
13. Energising sequence:

Close isolator first, then close CB

35 Phase 8 Self-Test

Answer these without seeing notes:

1. What is protection in power system?

2. Why is protection necessary?
3. What is a fuse?
4. What is fuse element?
5. Define current rating and fusing current.
6. What is fusing factor?
7. What is prospective current?
8. What is pre-arcing time?
9. What is arcing time?
10. What is HRC fuse?
11. Why is silica powder used in HRC fuse?
12. What is a protective relay?
13. What is the job of a circuit breaker?
14. What is an isolator?
15. Why should isolator not be opened on load?
16. Compare fuse and circuit breaker.
17. Compare circuit breaker and isolator.

Common Mistake

Do not write that relay directly breaks the main circuit. Correct statement:

Relay detects fault and circuit breaker interrupts fault current.

End of Phase 8

Next Phase:

Phase 9 – Substation and Busbar Arrangement

Substation classification, equipment, CT, PT, isolator, circuit breaker, lightning arrester, pole-mounted substation and busbar schemes.